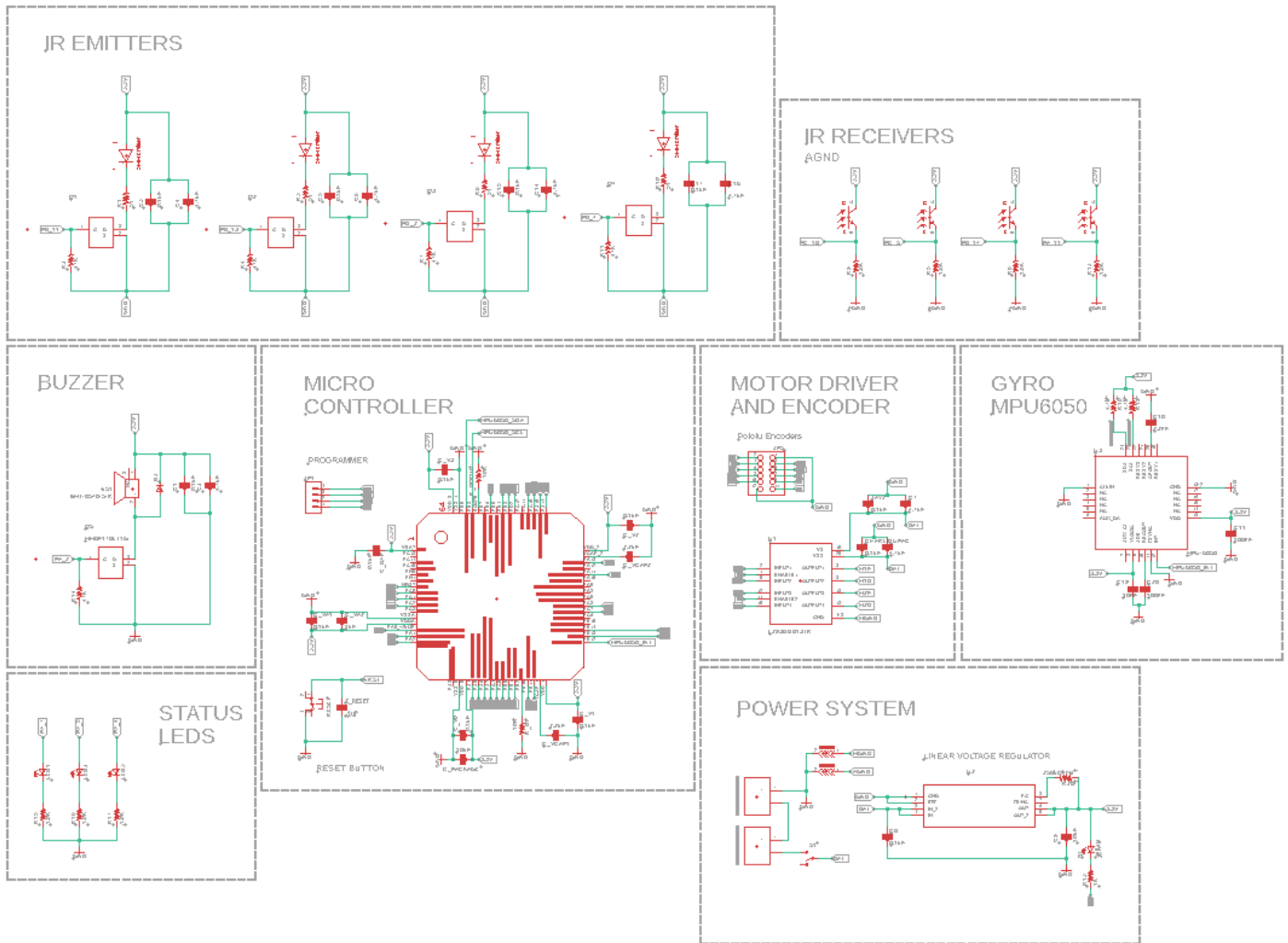


MICROMOUSE




SCHEMATIC



KEY SUMMARY


- 3-axis accelerometer and gyroscope (MPU6050) to measure speed and track the orientation of the mouse
- Status LEDs and a buzzer for easier debugging and interfacing with the microcontroller
- IR emitters and receivers to detect maze walls and corners
- Magnetic encoder to track the position of the mouse, and for precision turning and general maneuvering
- Dual H-bridge motor driver (L293DD) to change the direction of rotation of the brushed DC gearmotors
- Simple 3.3V LDO regulator (TPS76833Q) to power the microcontroller with minimal footprint
- On-board MCU (STM32F405RG) to run maze-solving algorithm and generic operations such as wall-detection and moving

BOARD (TOP & BOTTOM)

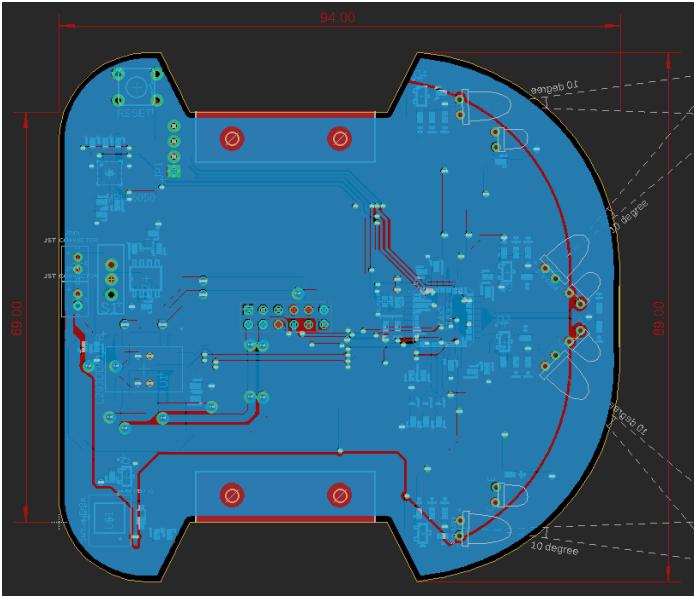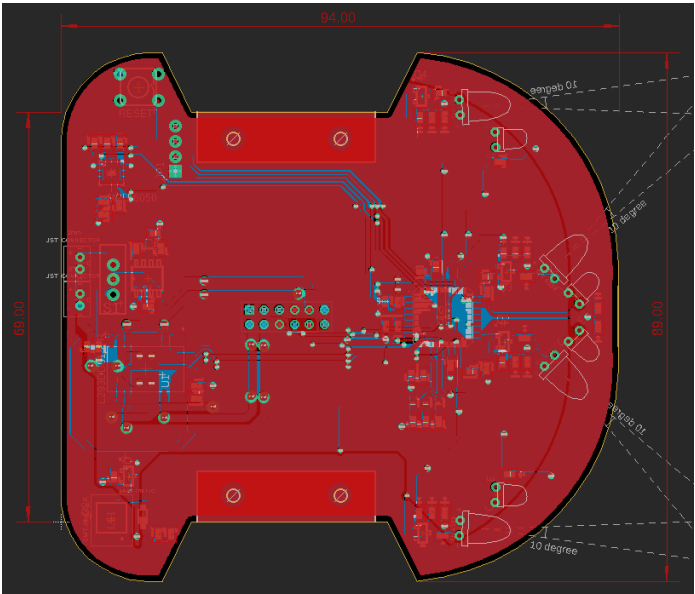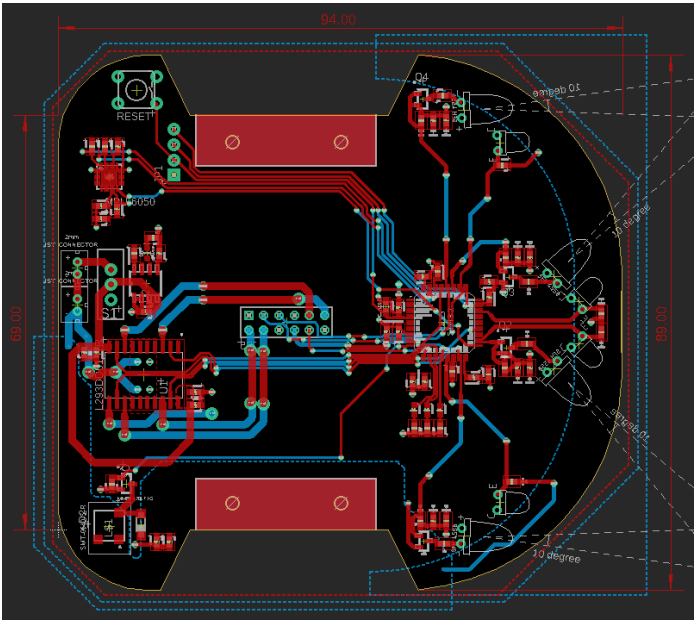


MINI QUADCOPTER

SCHEMATIC

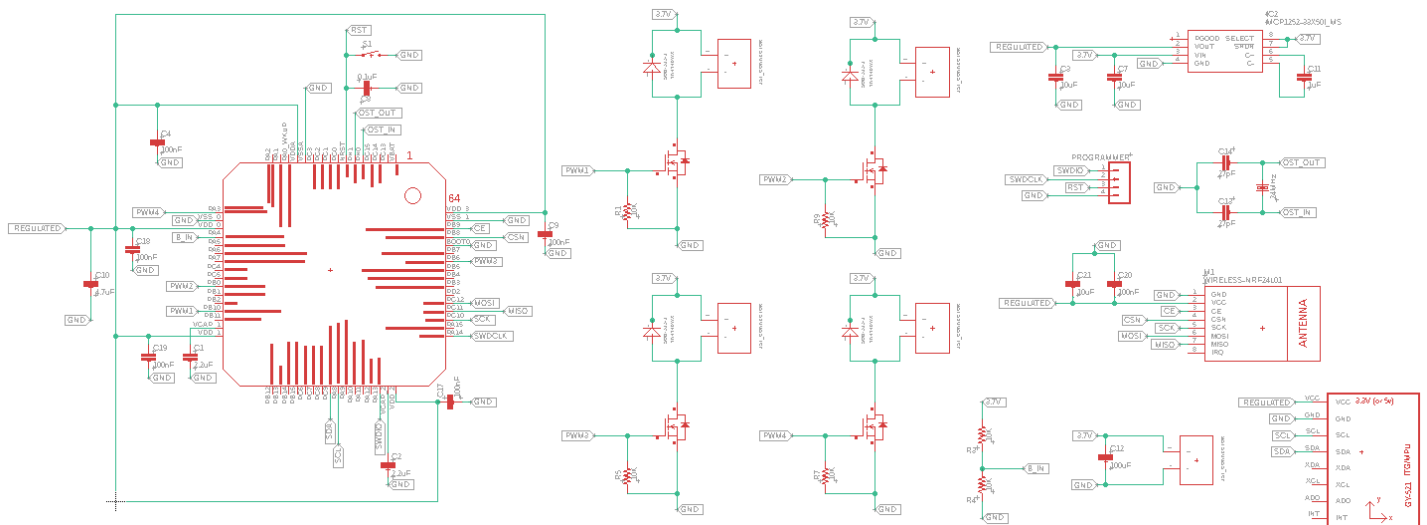




3D Model

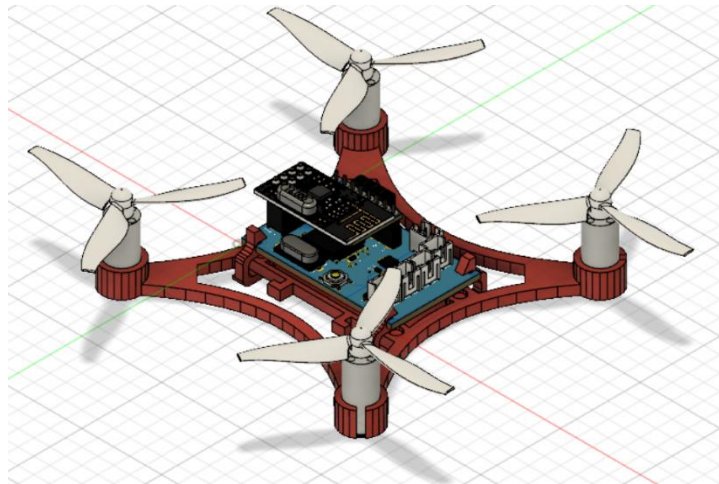

KEY SUMMARY


- 3-axis accelerometer and gyroscope (MPU6050) to track orientation of quadcopter for flight stability
- 2.4 GHz wireless transceiver (NRF24L01) to communicate with RC transmitter wirelessly
- Simple low-side drivers (BSS138) to drive 4 coreless DC motors
- External 24 MHz crystal oscillator (ABLS2) for accurate frequency and frequency stability
- 3.3V charge pump DC/DC converter (MCP1252) for low noise, higher efficiency, and a smaller footprint
- On-board MCU (STM32F405RG) to execute flight controller software code

BOARD (TOP & BOTTOM)

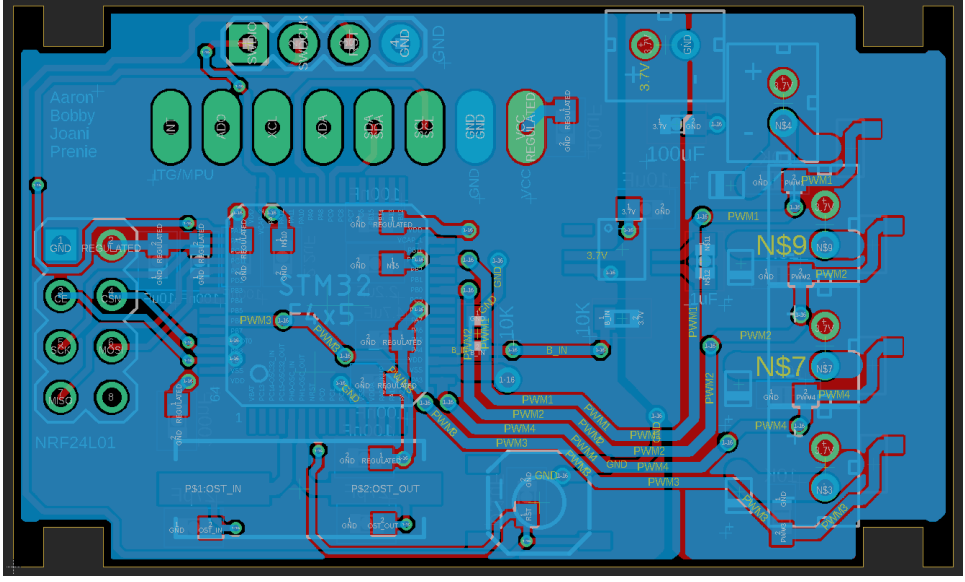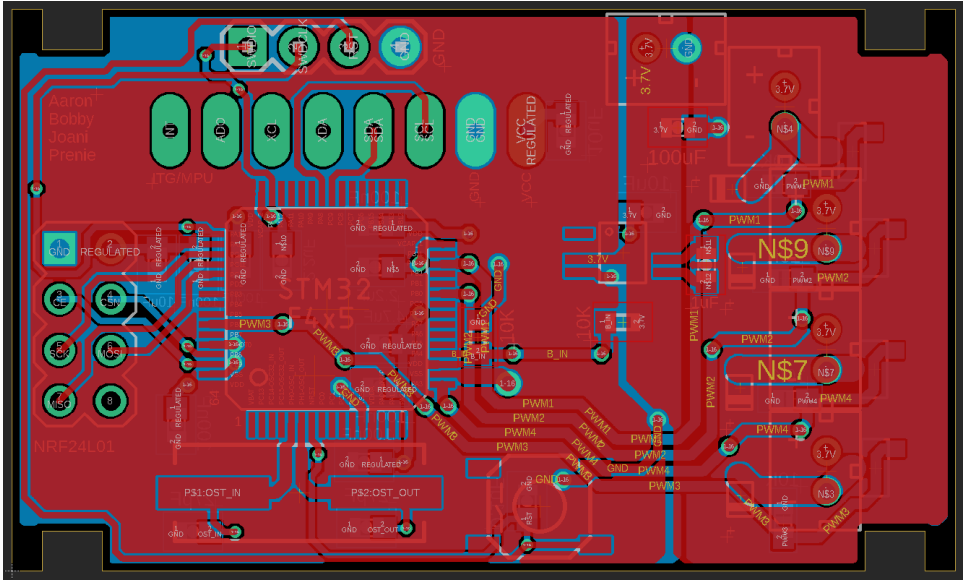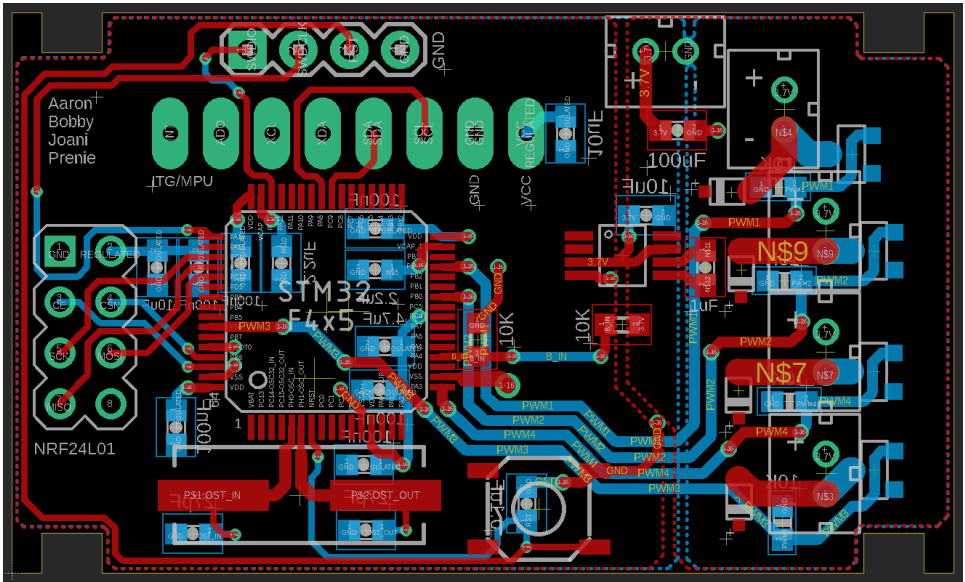

WEARABLE SWEAT SENSOR




SCHEMATIC

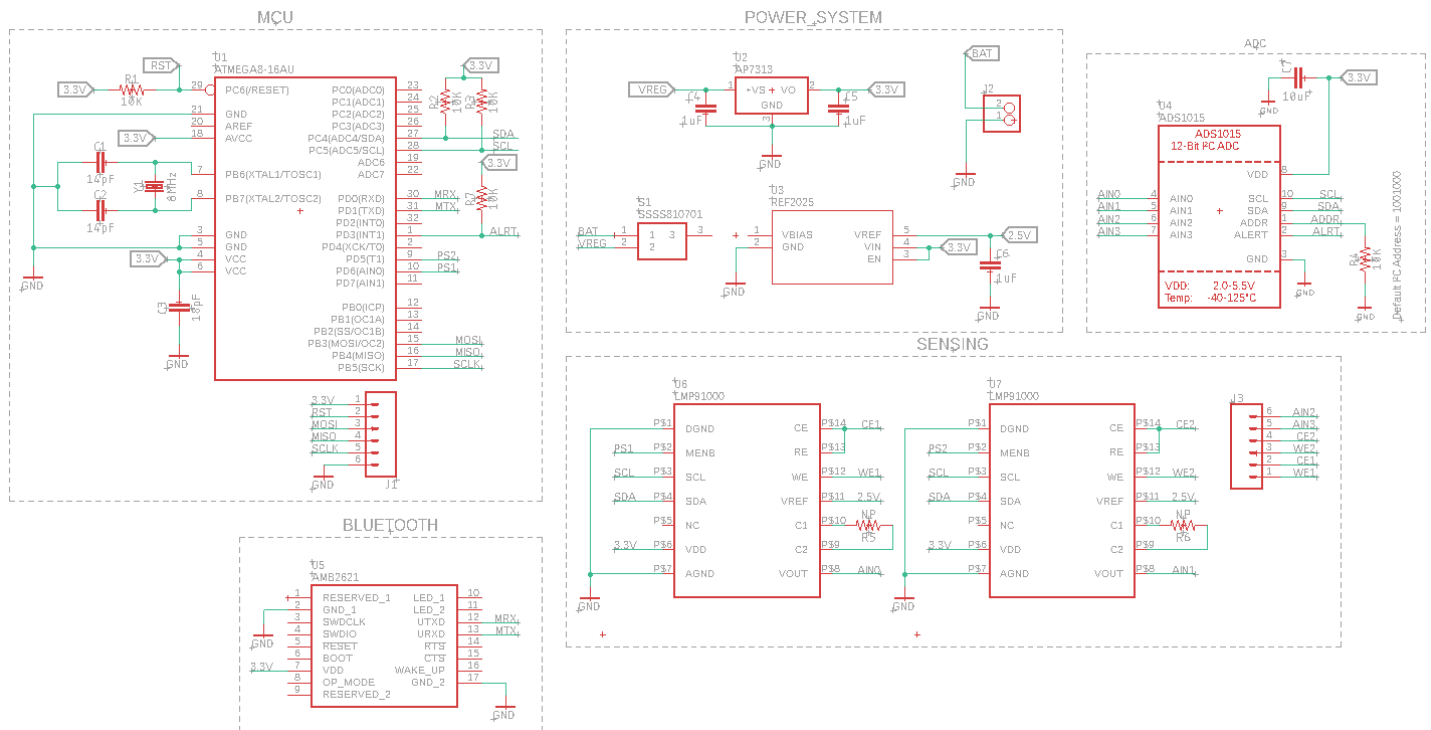

KEY SUMMARY

- Fully integrated wearable sensor arrays for multiplexed *in-situ* sweat analysis
- 12-bit ADC (ADS1015) for precise measurements of trace amounts of sweat metabolites and electrolytes
- AFE potentiostats (LMP91000) for low power electrochemical sensing
- BLE 4.2 module (AMB2621) to enable wireless functionality with a mobile application
- Simple 3.3V LDO regulator (AP7313) to power the ADC, potentiostats, and the ATmega8 chip

BOARD (TOP & BOTTOM)

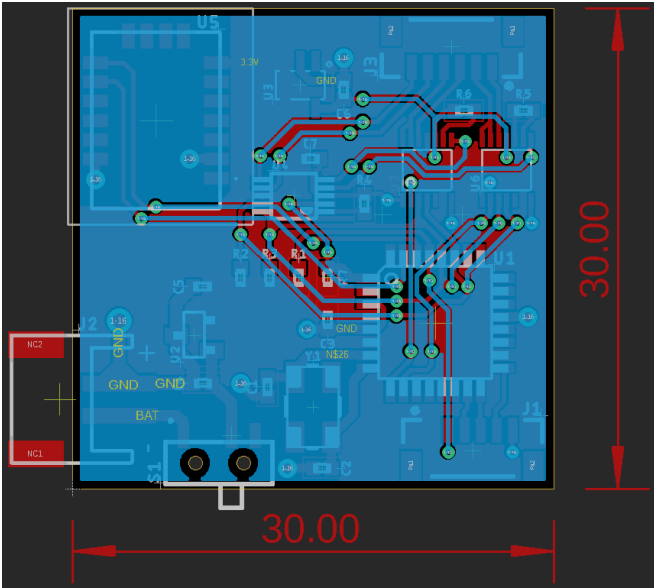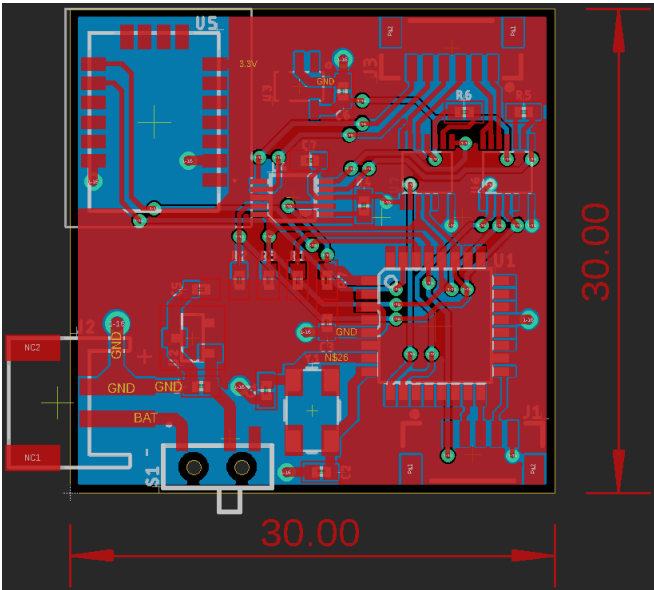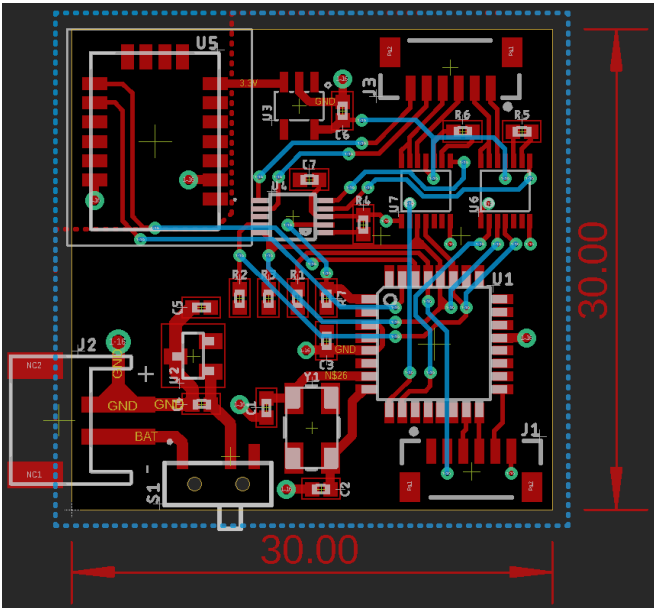

**A 1.25 GHz 0.23 pJ
4-bit Absolute-Value Detector
for use in Neural Spike Sorting**

Aaron Lim

Prathyush Sivakumar




Design Summary

- ◆ Optimized 3-Bit Ripple-Carry Adder + Comparator, Static CMOS + Pass Transistor Logic (PTL)
- ◆ Moderate Area, Fast, Compact Design (Extra Room for Additional Logic)


***VDD = 1V**

Schematic	Layout size	Energy	Verification
$t_{p_x0 \rightarrow OUT} = 778 \text{ ps}$	X = 21.6 μm	Sch E = 204 fJ	Func: Y / N
$t_{p_x1 \rightarrow OUT} = 620 \text{ ps}$	Y = 19.5 μm	Layout E = 226 fJ	DRC: Y / N
$t_{p_x2 \rightarrow OUT} = 524 \text{ ps}$	A = 421.2 μm^2		LVS: Y / N
$t_{p_x3 \rightarrow OUT} = 599 \text{ ps}$	AR = 1.11		
$t_p = 778 \text{ ps}$			

Critical Path Analysis

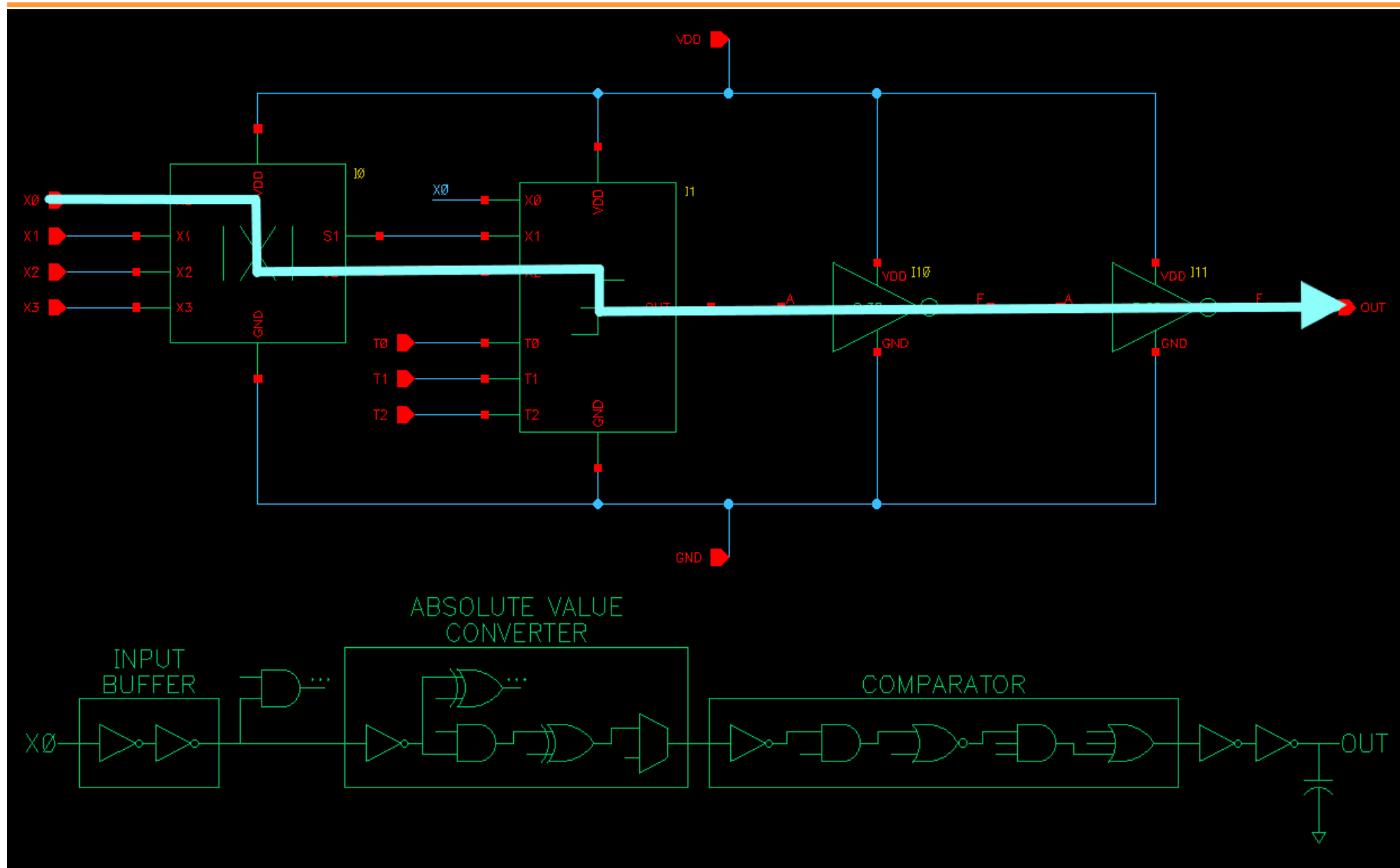

Design Optimization

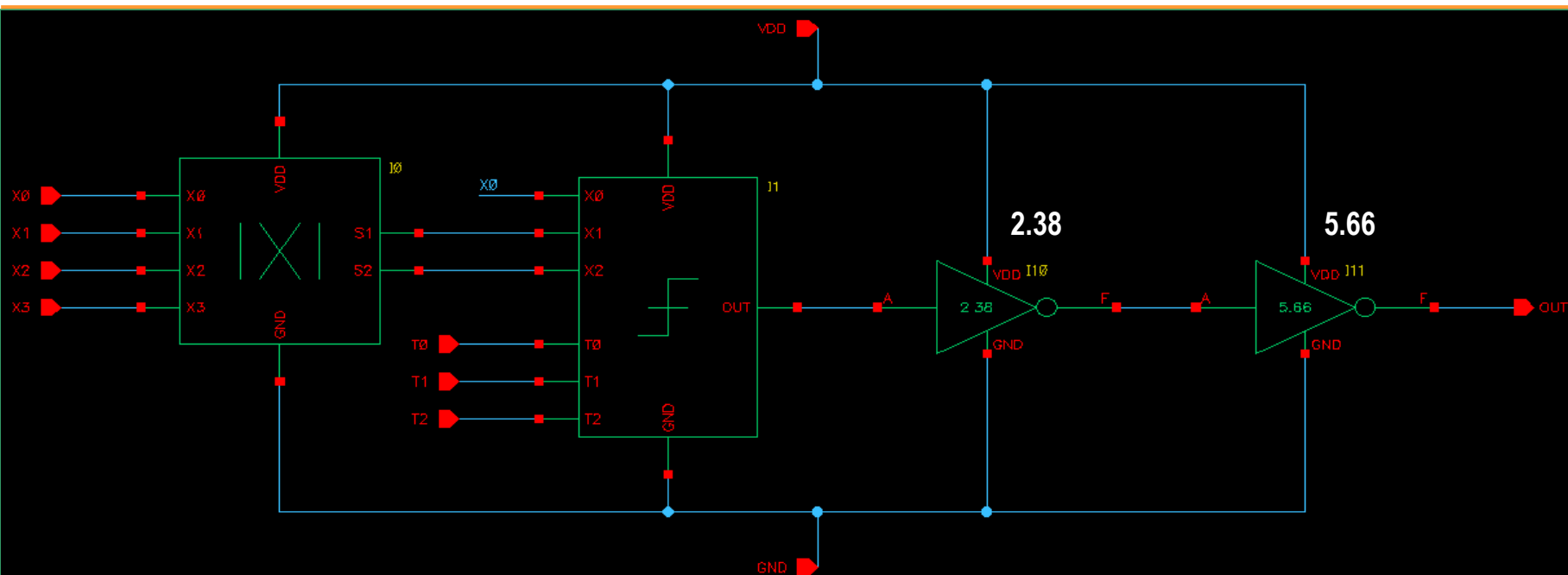

- ◆ Isolated high fan-out using sized output buffer (i.e. two sized inverters) to minimize delay
- ◆ Simplified adder design by realizing classes of inputs. Resulted in much fewer logic gates
- ◆ Used PTL for MUX and XOR to reduce no. of transistors to implement logic
- ◆ Used only 2 1-bit MUXes by realizing that MSB and LSB are always the same

Functionality Check (Schematic)




Absolute-Value Detector Layout

2 Highlight critical path

1 Show layout

6 Anything else
Density:
88.2%

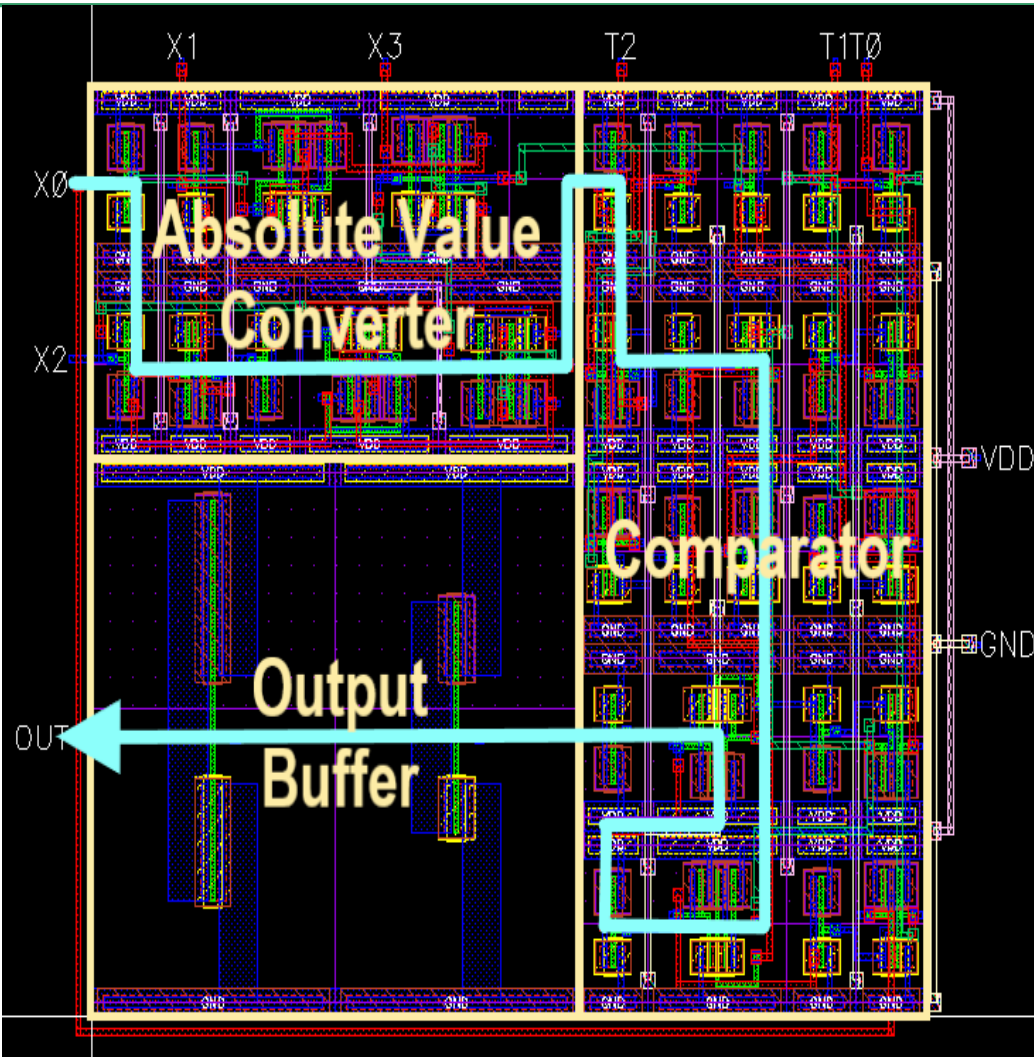

3 Indicate size

$Y = 19.5\mu\text{m}$

$X = 21.6\mu\text{m}$

4 AR, Area
Aspect ratio:
1.11

Area:
 $421.2\mu\text{m}^2$

5

Discussion

◆ **Three most important features of your design**

- Isolation of large load capacity / high fan-out using sized output buffer
- PTL for MUX and XOR for reduced power consumption
- Compact and systematic layout with room for extra logic

◆ **Given another chance, 3 things you would do different**

- Perform further sizing analysis to achieve optimum propagation delay
- Optimize critical path by reordering transistors